

MEASUREMENT OF POWER

MEASUREMENT OF POWER:

Aim of the experiment:

Three phase power measurement by two wattmeter method.

Theory:

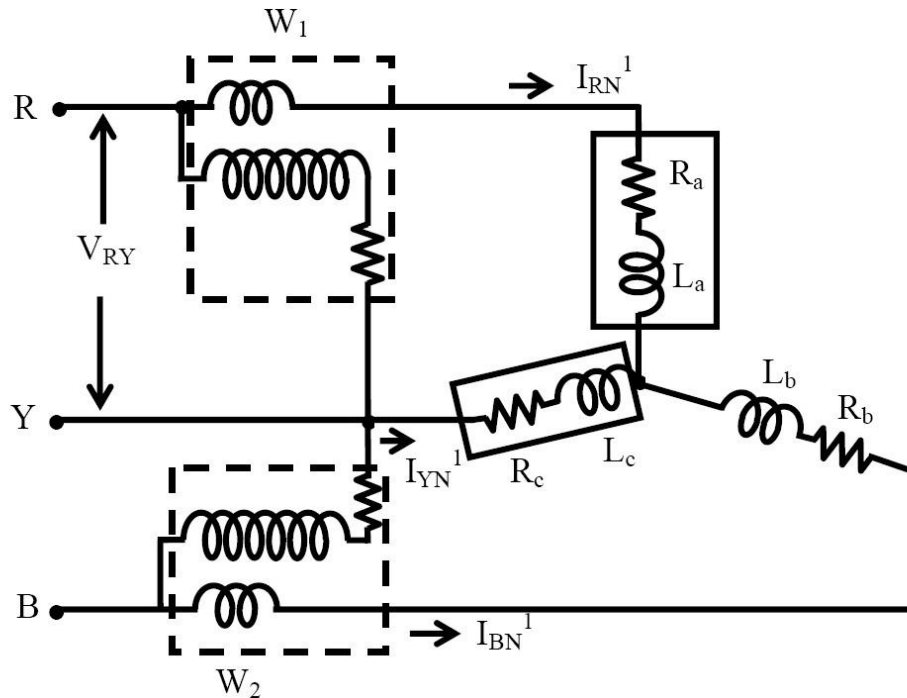


Fig 1: Connection diagram for three phase power measurement using two wattmeter method

The connection diagram for the measurement of power in three phase power measurement circuit using two wattmeter's method is shown in figure 1. This is irrespective of the circuit connection star or delta. The circuit may be taken as balanced or unbalanced one, balanced type being only a special case. Please note the connection of two wattmeter's. The current coil of the wattmeter's 1 and 2 in series with R and B phase with the pressure voltage coils being connected across R-Y and B-Y respectively. Y is the third phase in which no current coil is connected.

If star connected circuit is taken as an example the total instantaneous power consumed in the circuit is,

$$W = I_{RN} * V_{RN} + I_{YN} * V_{YN} + I_{BN} * V_{BN} \dots (1)$$

Each of the terms in the above expression equation (1) is the instantaneous power consumed by the phases. From the connection diagram, the circuit in and the voltages across the respective (current, pressure or voltage) coils in the wattmeter, W1 are I_{RN} and.

$$V_{RY} = V_{RN} - V_{YN}$$

So, the instantaneous power measured by the wattmeter W1 is.

$$W_1 = I_{RN} * V_{RY}$$

Similarly the instantaneous power measured by the wattmeter W2 is .

$$W_2 = I_{BN} * V_{BY} = I_{BN} * (V_{BN} - V_{YN})$$

Some of the two readings as given above is,

$$\begin{aligned} W_1 + W_2 &= I_{RN}(V_{RN} - V_{YN}) + I_{BN}(V_{BN} - V_{YN}) \\ &= I_{RN}V_{RN} + I_{BN}V_{BN} - V_{YN}(I_{RN} + I_{BN}) \dots (2) \end{aligned}$$

$$\text{and } I_{RN} + I_{BN} + I_{YN} = 0$$

applying in equation (2),

$$W_1 + W_2 = I_{RN}V_{RN} + I_{BN}V_{BN} + V_{YN}I_{YN} \dots (3)$$

Equation (1) is compared with equation (3) to give the total instantaneous power consumed in the circuit . They are found to be same. The phasor diagram of three phase balanced star connected circuit is shown in figure 2.

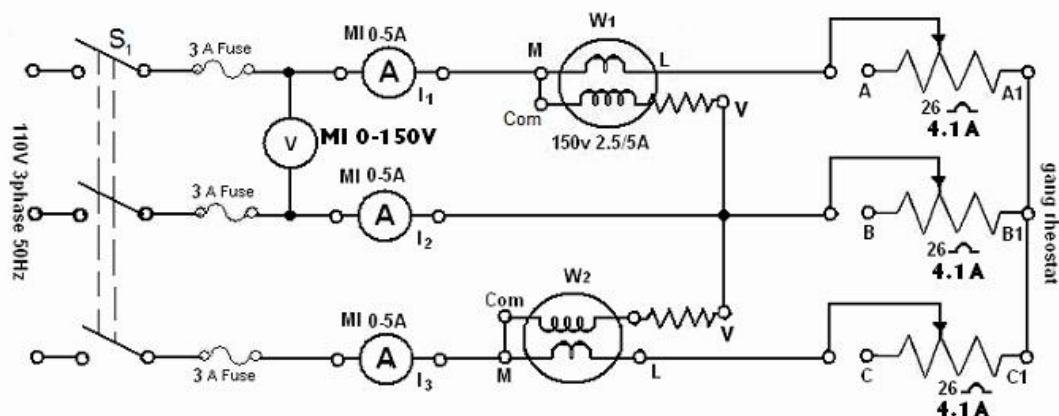


Fig. 1. Three phase power measurement circuit under balance condition

1. Connect the circuit as shown in Fig. 1.
2. Adjust the ganged rheostat for the maximum resistance.
3. Switch on the supply.
4. Close switch S1.
5. Read the meters to obtain VL, I1, I2 and I3. Note the wattmeter reading W1 and W2 (Note the multiplying factor on the wattmeter).
6. Vary the load resistance and obtain at least five sets of observations, the current should not exceed the limit (4.1 A).

UNBALANCED LOAD :

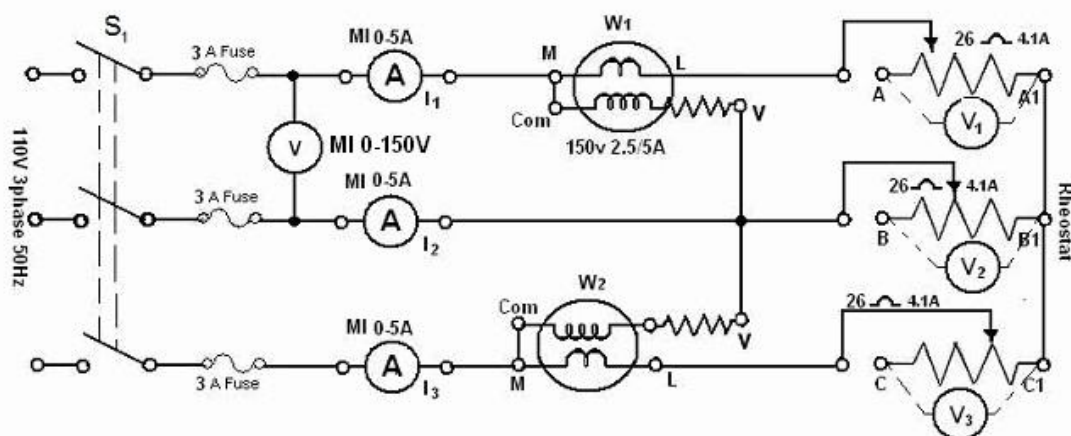



Fig. 2. Three phase power measurement circuit under unbalance condition

- Connect the circuit as shown in Fig. 2.
- Replace the ganged rheostat by three separate rheostats of $26\ \Omega$, $4.1\ \text{A}$ and connect in a star.
- Adjust the three rheostats at the maximum values.
- Switch on the supply and set the autotransformer to $110\ \text{V}$.
- Close switch S_1 and take five sets of observation for different rheostat settings such that the reading of I_1 , I_2 and I_3 in each set is appreciably different to create unbalanced loading condition. The current should not exceed the limits in each arm.


SIMULATION

BALANCED:


Case 1:

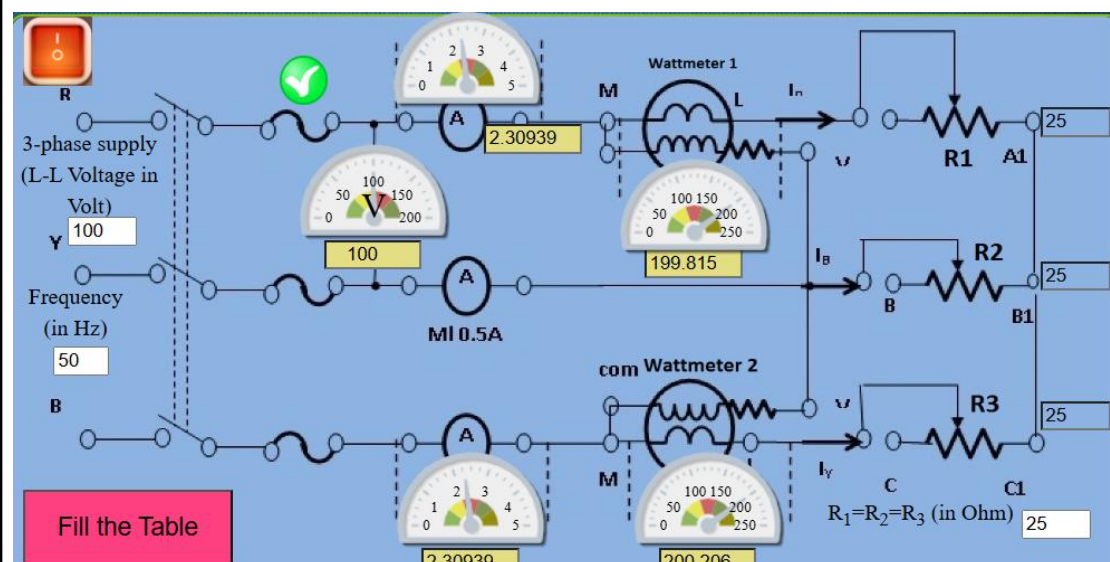


Case 2:

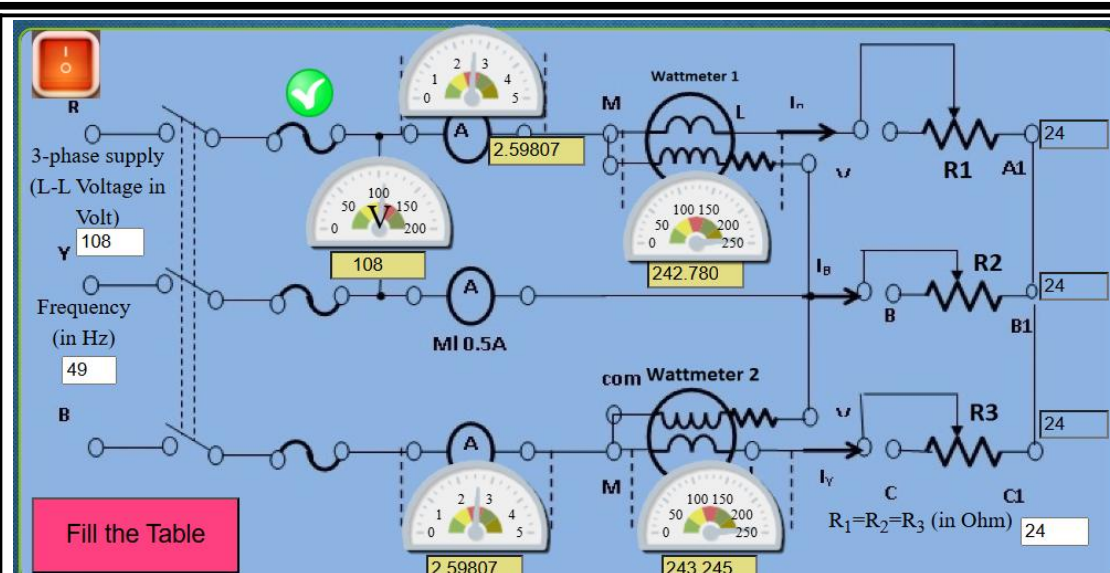


Case 3:

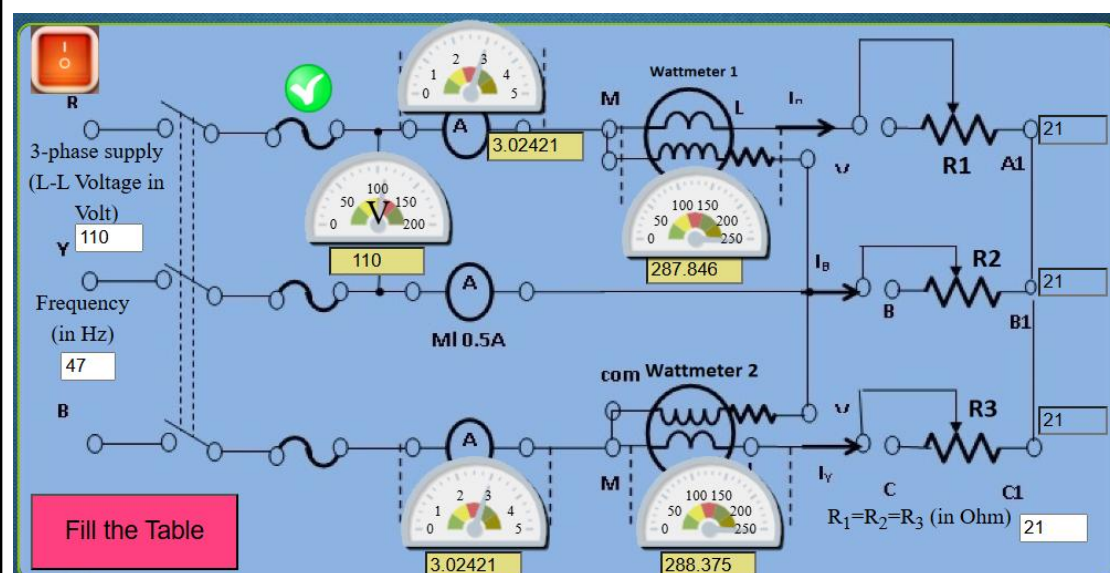

Case 4:

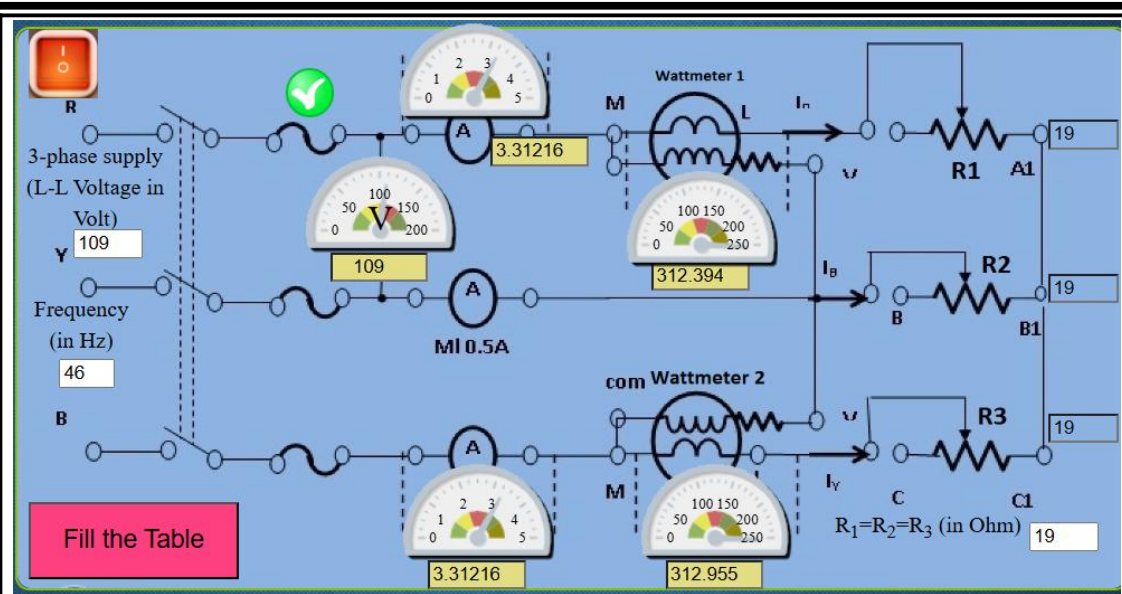

Case 5:

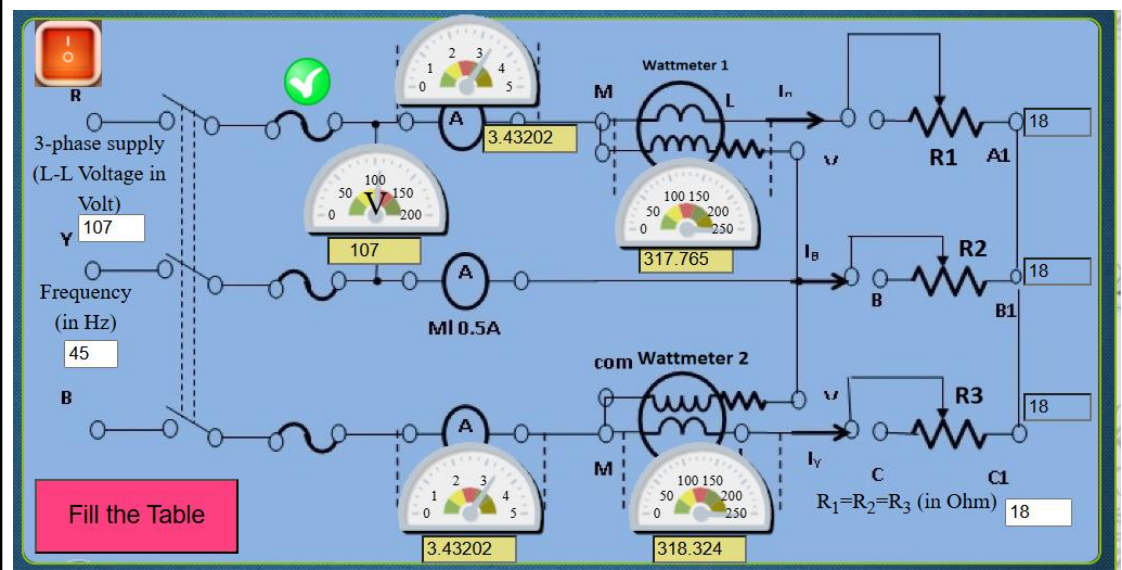


Tabulation for Balanced load:


| Observation Table | | | | | | | | | | | |
|---------------------------|----------|-------------|---------------------|----------|-------------|---------------------|-------------|-----------|-----------|--------------------------|------------------------------------|
| Serial no. of Observation | V_{RY} | I_R (Amp) | $\cos(V_{RY}, I_R)$ | V_{BY} | I_B (Amp) | $\cos(V_{BY}, I_B)$ | I_3 (Amp) | W_1 | W_2 | W_C (Calculated power) | W_M (Measured Power= W_1+W_2) |
| 1st | 100 | 2.3093977 | 0.8652280 | 100 | 2.3093977 | 0.8669190 | 2.3093977 | 199.81557 | 200.20600 | 399.99885 | 400.02160 |
| 2nd | 108 | 2.5980720 | 0.8652440 | 108 | 2.5980720 | 0.8669021 | 2.5980720 | 242.78060 | 243.24560 | 485.99860 | 486.02637 |
| 3rd | 110 | 3.0242118 | 0.8652780 | 110 | 3.0242118 | 0.8668684 | 3.0242118 | 287.84654 | 288.37530 | 576.18901 | 576.22187 |
| 4th | 109 | 3.3121630 | 0.8652950 | 109 | 3.3121630 | 0.8668516 | 3.3121630 | 312.39410 | 312.95570 | 625.31427 | 625.34990 |
| 5th | 107 | 3.4320220 | 0.8653120 | 107 | 3.4320220 | 0.8668347 | 3.4320220 | 317.76570 | 318.32461 | 636.05408 | 636.09030 |

Unbalanced:


Case 1:

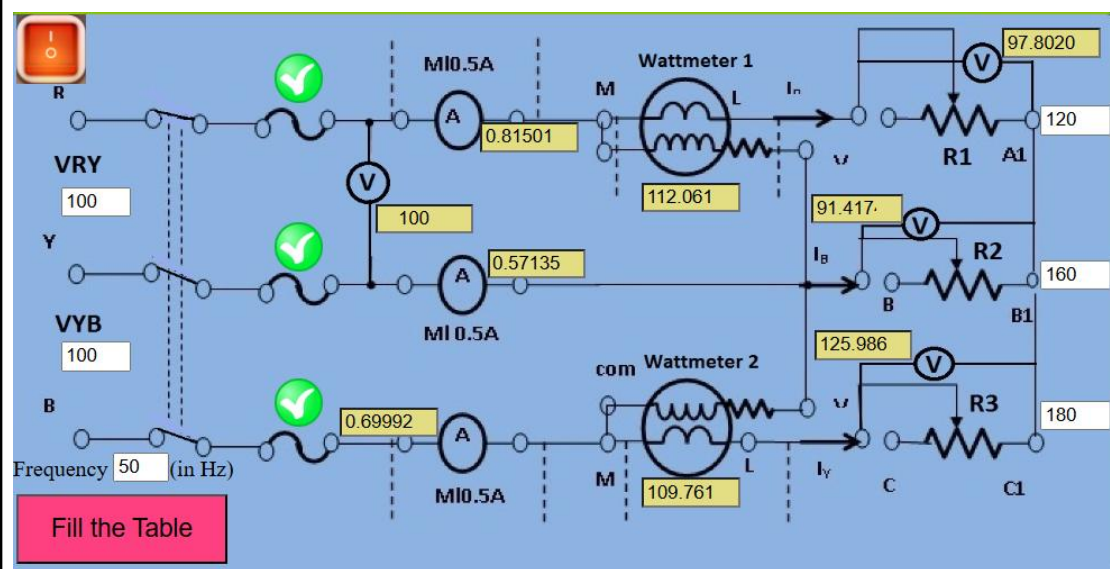

Case 2:

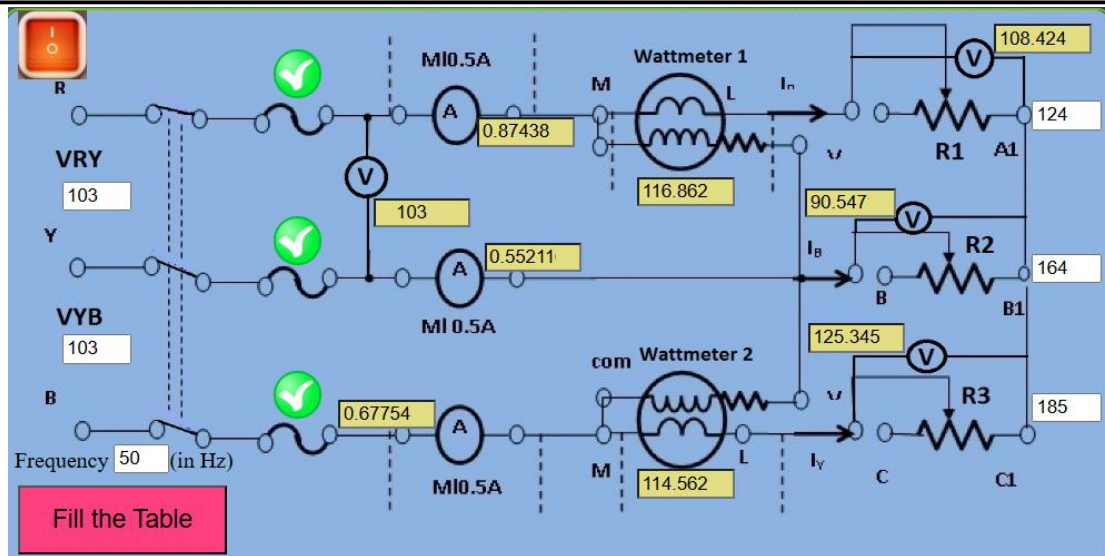

Case 3:

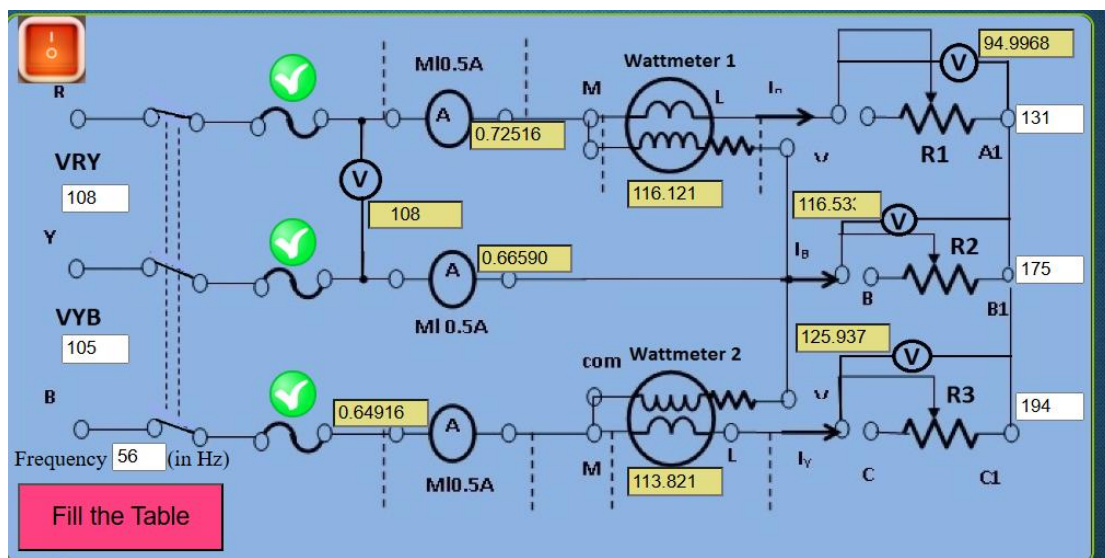

Case 4:

| Observation Table | | | | | | | | | | |
|---------------------------|-----------|-----------|-----------|-------------|-------------|-------------|--------------------------|-----------|-----------|------------------------------------|
| Serial no. of Observation | V_R | V_Y | V_B | I_R (Amp) | I_Y (Amp) | I_B (Amp) | W_C (Calculated power) | W_1 | W_2 | W_M (Measured Power= W_1+W_2) |
| 1st | 97.802081 | 91.417450 | 125.98662 | 0.8150173 | 0.5713590 | 0.6999256 | 220.12385 | 112.06192 | 109.76192 | 221.82385 |
| 2nd | 108.42402 | 90.547178 | 125.34560 | 0.8743873 | 0.5521169 | 0.6775438 | 229.72436 | 116.86218 | 114.56218 | 231.42436 |
| 3rd | 94.996842 | 116.53391 | 125.93768 | 0.7251667 | 0.6659081 | 0.6491633 | 228.24356 | 116.12178 | 113.82178 | 229.94356 |
| 4th | 128.93946 | 105.10327 | 153.88519 | 0.9694696 | 0.6448053 | 0.7618078 | 310.00500 | 157.00250 | 154.70250 | 311.70500 |
| 5th | 131.44323 | 125.80938 | 121.10700 | 1.3014181 | 1.1334178 | 1.1425188 | 452.02425 | 228.01212 | 225.71212 | 453.72425 |

RESULT:

Thus the Measurement of Power is Simulated and validated